

(*)	Sequential Logic
^	<p>IMMEDIATELY AFTER a circuit is CLOSED, while the initial PROPAGATIONS have NOT completed, the values on the wires (except for those which are DIRECTLY fixed to 0's/1's) will be FLOATING (at 0, 1 or somewhere between 0 &amp; 1, or oscillating among 0, 1 and somewhere between 0 &amp; 1), including the MASTER-CLOCK generator.</p> <p>A MASTER-CLOCK generator is a TIMING device which generates a PERIODIC train of CLOCK PULSES, i.e. a signal which goes to 0 to 1 to 0 to 1 and so forth PERIODICALLY.</p> <p>In GENERAL, for EVERY logic gate, its OUTPUT will become 0/1 only AFTER its INPUT(s) become(s) 0/1 (including FLOATING at 0/1) and AFTER its PROPAGATION DELAY.</p> <p>Also, if its INPUT(s) later become FLOATING somewhere between 0 &amp; 1, then AFTER its PROPAGATION DELAY, its OUTPUT will also become FLOATING (at 0, 1 or somewhere between 0 &amp; 1, or oscillating among 0, 1 and somewhere between 0 &amp; 1) if its OUTPUT is NOT being driven by some OTHER component.</p>
	<div data-bbox="210 1243 469 1426" data-label="Diagram"> <pre> graph LR     A --&gt; OR[OR]     B --&gt; OR     OR --&gt; Q </pre> </div> <p>For eg., if the PROPAGATION DELAY of this OR gate is 20 ns, if A &amp; B are FIXED to 1's, and if the circuit is completed at <math>t = 0</math>, then Q will be FLOATING from <math>t = 0</math> to <math>t = 20</math> and will be 1 AFTER <math>t = 20</math>.</p>
	<p>For eg., if ONE input of an OR gate becomes 1 (including FLOATING at 1), then after its PROPAGATION delay, its OUTPUT will become 1 IRRESPECTIVE of the OTHER input (even if that OTHER input is FLOATING (at 0, 1 or somewhere between 0 &amp; 1, or oscillating among 0, 1 and somewhere between 0 &amp; 1)).</p> <p>However, if ONE input of an OR gate becomes 0 (including FLOATING at 0) and the OTHER input becomes FLOATING somewhere between 0 &amp; 1, or if BOTH inputs become FLOATING somewhere between 0 &amp; 1, then after its PROPAGATION delay, its OUTPUT will become FLOATING (at 0, 1 or somewhere between 0 &amp; 1, or oscillating among 0, 1 and somewhere between 0 &amp; 1) if its OUTPUT is NOT being driven by some OTHER component.</p>

An INPUT of a LOGIC GATE will be FLOATING (at 0, 1 or somewhere between 0 & 1, or oscillating among 0, 1 and somewhere between 0 & 1) if it is DISCONNECTED, if the OUTPUT which is driving this INPUT is FLOATING (at 0, 1 or somewhere between 0 & 1, or oscillating among 0, 1 and somewhere between 0 & 1), etc.

A FLOATING value MAY at times float at 0/1, but an ACTUAL 0/1 will REMAIN constant until it gets CHANGED (after, for eg., the corresponding PROPAGATION DELAY(s) due to the INPUTS getting changed), whereas a FLOATING value MAY get changed ARBITRARILY. Thus, an OSCILLATING signal (for eg., from a MASTER-CLOCK generator) oscillating between 0 & 1 oscillates due to, for eg., INPUTS getting changed, which is DIFFERENT from a FLOATING value, which MAY oscillate among 0, 1 and somewhere between 0 & 1 ARBITRARILY.


The outputs of a COMBINATIONAL circuit at ANY instant of time are ENTIRELY dependent upon the inputs present at THAT time, taking into account the PROPAGATION delays.

However, in a SEQUENTIAL circuit, MEMORY elements are present as well.

The information stored in the MEMORY elements at any given time defines the present STATE of the sequential circuit.

The external OUTPUTS and the next STATE of a sequential circuit are both functions of the external INPUTS and the present STATE.

 Thus, a sequential circuit is specified by a time sequence of EXTERNAL INPUTS, EXTERNAL OUTPUTS and STATES.



A SYNCHRONOUS sequential circuit is a system whose behaviour can be defined from the knowledge of its signals at DISCRETE instants of time.

The behaviour of an ASYNCHRONOUS sequential circuit depends upon the ORDER in which its input signals change and can be affected at ANY instant of time.

So, the behaviour of an ASYNCHRONOUS sequential circuit CANNOT be defined at DISCRETE instants of time.

The MEMORY elements used in ASYNCHRONOUS sequential circuits are TIME-DELAY devices, whose memory capability is due to the FINITE amounts of time it takes for signals to PROPAGATE through devices. Instead of using physical time-delay devices, LOGIC GATES may also be used to produce the SAME effect due to their internal PROPAGATION delays.

Thus, an ASYNCHRONOUS sequential circuit may be regarded as a COMBINATIONAL circuit with FEEDBACK. Because of the feedback among logic gates, an asynchronous sequential circuit may, at times, become UNSTABLE.

In a SYNCHRONOUS sequential circuit, signals may affect the MEMORY elements only at DISCRETE instants of time.

One way of achieving this goal is by using a MASTER-CLOCK generator, and a circuit which uses a MASTER-CLOCK generator is known as a CLOCKED SYNCHRONOUS sequential circuit.

In practical circuits, the MEMORY elements are affected ONLY with the ARRIVAL of a pulse, i.e. IMMEDIATELY after the clock goes from 0 to 1 (i.e. during the POSITIVE edge transition) or from 1 to 0 (i.e. during the NEGATIVE edge transition), depending upon the implementation, and NOT during the ENTIRE time the clock stays at 1 or 0. Such circuits are called EDGE-TRIGGERED CLOCKED SYNCHRONOUS sequential circuits, and the MEMORY elements used in such circuits are called FLIP-FLOPS.

The basic difference between a LATCH and a FLIP-FLOP is that a LATCH is LEVEL-SENSITIVE, i.e. the outputs of a LATCH respond to new inputs AT ALL TIMES, whereas a FLIP-FLOP is EDGE-TRIGGERED, i.e. the outputs of a FLIP-FLOP respond to new inputs ONLY during the positive/negative EDGE TRANSITIONS of the clock.

Hence, LATCHES are examples of ASYNCHRONOUS sequential circuits, whereas FLIP-FLOPS are examples of EDGE-TRIGGERED CLOCKED SYNCHRONOUS sequential circuits. Adding a clock input to a latch DOESN'T make it a FLIP-FLOP, as its outputs will respond to new inputs during the ENTIRE time the clock stays at 1, and rather makes it a GATED LATCH, which is an example of a LEVEL-SENSITIVE CLOCKED SYNCHRONOUS sequential circuit.

Note that 'DURING an edge transition' means 'IMMEDIATELY AFTER the clock goes from 0 to 1 or from 1 to 0', depending upon the implementation.

^	A LATCH / FLIP-FLOP is a memory element (CELL) capable of storing 1 BIT of information.
	Each latch / flip-flop has 2 outputs, Q & Q'.
	When $Q = 1$ & $Q' = 0$ , the state is SET, and when $Q = 0$ & $Q' = 1$ , the state is CLEAR.
	In the beginning, when power is turned on, a latch / flip-flop GENERALLY results in either a STABLE SET state or a STABLE RESET state.
	However, it MAY also result in an OSCILLATING state.
	Thus, in the beginning, GENERALLY, every latch / flip-flop is CLEARED, for eg., by using DIRECT CLEAR inputs, BEFORE the normal operation of the computer begins.
^	For every CLOCKED SYNCHRONOUS memory element (i.e. GATED LATCH / FLIP-FLOP),
	1. The SETUP time is defined as the DURATION of time for which the input(s) must be kept CONSTANT while CP is at 0 IMMEDIATELY BEFORE CP gets changed from 0 to 1.
	2. The HOLD time is defined as the DURATION of time for which the input(s) must be kept CONSTANT while CP is at 1 IMMEDIATELY AFTER CP gets changed from 0 to 1.
	For eg., if the DURATION of a clock cycle is 20 units, with the clock staying at 1 & 0 for 10 units each and the clock transitioning from 0 to 1 at $t = 20 T$ , where T is an integer, and if the SETUP & HOLD times of a flip-flop are 2 units & 1 unit, respectively, then the input(s) must be kept CONSTANT from $t = (20 T - 2)$ to $t = (20 T + 1)$ .
	It should be noted that the ARRIVAL of the input(s) EXACTLY at $t = (20 T - 2)$ and the CHANGING of the inputs EXACTLY at $t = (20 T + 1)$ may work IDEALLY, but MAY or MAY NOT work in REAL-WORLD circuits. So, the input(s) must arrive slightly BEFORE $t = (20 T - 2)$ and must be allowed to change only slightly AFTER $t = (20 T + 1)$ .

In REAL-WORLD circuits, the duration of a clock cycle is MUCH MORE than this.

In GENERAL, the data to be loaded into truly POSITIVE edge-triggered flip-flops in the NEXT clock cycle arrive at the inputs while the clock is 0, while the clock was previously 1, etc., such that the SETUP time constraint is NOT violated.

Then, the data get loaded into those AFTER the clock gets changed to 1 in the NEXT clock cycle.

Finally, the inputs may get changed while the clock is still 1, after the clock gets changed to 0, etc., such that the HOLD time constraint is NOT violated.

These changed inputs MAY or MAY NOT correspond to the data to be loaded in the future.  
[Similarly for truly NEGATIVE edge-triggered flip-flops]

Since a latch / flip-flop has 2 STABLE states, therefore it is aka a BISTABLE MULTIVIBRATOR.

^ For some reason, the book calls the gated SR, D, JK and T latches as flip-flops, even though their outputs may change the ENTIRE time the clock is at 1, and NOT ONLY during EDGE TRANSITIONS of the clock.

^ SR Latch (aka DIRECT-COUPLED RS Flip-Flop, even though it is technically a LATCH)